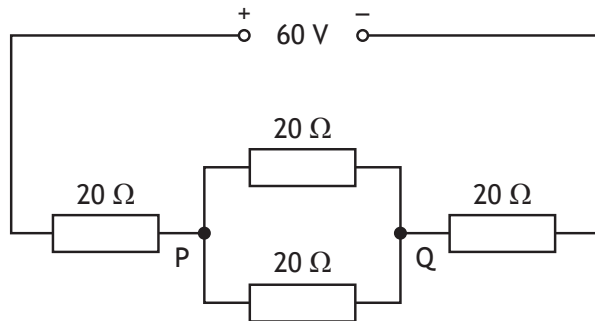


23. Four resistors each of resistance $20\ \Omega$ are connected to a 60 V supply of negligible internal resistance as shown.



The potential difference across PQ is

- A 12 V
- B 15 V
- C 20 V
- D 24 V
- E 30 V .