

Question			Expected response	Max mark	Additional guidance
12.	(a)	(i)	$\left(\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} \right)$ $\left(\frac{1}{R_T} = \frac{1}{16} + \frac{1}{16} \right)$ $R_T = 8(\Omega) \quad (1)$ $R = ((8+16) =) 24(\Omega) \quad (1)$ $V = IR \quad (1)$ $V = 0.38 \times 24 \quad (1)$ $V = 9.1 \text{ V} \quad (1)$	5	Accept: 9, 9.12, 9.120 24 (Ω) anywhere 2 marks $V = IR$ anywhere - 1 mark Alternative methods 2 marks for 24 (Ω) anywhere 1 mark for all relationships 1 mark for all substitutions 1 mark for final answer
		(ii)	$E = V + Ir \quad (1)$ $12 = 9.1 + (0.38 \times r) \quad (1)$ $r = 7.6 \Omega \quad (1)$	3	Or consistent with a(i)* Accept: 8, 7.63, 7.632 *If $V = 12 \text{ V}$ then max 1 mark for relationship. Alternative method: $E = I(R + r) \quad (1)$ $12 = 0.38(24 + r) \quad (1)$ $r = 7.6 \Omega \quad (1)$ For this method accept: 8, 7.58, 7.579 for 'lost volts' accept: $V = Ir$ $V = IR$

Question			Expected response	Max mark	Additional guidance
12.	(a)	(iii)	$P = I^2 R$ (1) $P = 0.38^2 \times 7.6$ (1) $P = 1.1 \text{ W}$ (1)	3	Or consistent with (a)(i) and/or(a)(ii) Accept: 1, 1.10, 1.097 Accept: $P = I^2 r$ Alternative methods: $P = IV$ (1) $P = 0.38 \times (12 - 9.1)$ (1) $P = 1.1 \text{ W}$ (1) OR $P = \frac{V^2}{R}$ (1) $P = \frac{(12 - 9.1)^2}{7.6}$ (1) $P = 1.1 \text{ W}$ (1)
	(b)		(Power dissipated) less than (1) (Total circuit resistance increases), current decreases, internal resistance stays the same (1)	2	MUST JUSTIFY Accept: current decreases, and lost volts decreases. lost volts decreases, and internal resistance stays the same.