

16. The power dissipated in a $120\ \Omega$ resistor is $4.8\ \text{W}$.

The current in the resistor is

- A $0.020\ \text{A}$
- B $0.040\ \text{A}$
- C $0.20\ \text{A}$
- D $5.0\ \text{A}$
- E $25\ \text{A}$.

[Turn over