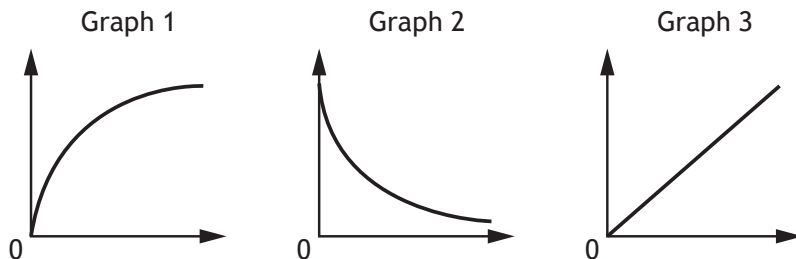


25. A student carries out three experiments to investigate the charging of a capacitor using a DC supply.

The graphs obtained from the experiments are shown.



The axes of the graphs have not been labelled.

Which row in the table shows the labels for the axes of the graphs?

	<i>Graph 1</i>	<i>Graph 2</i>	<i>Graph 3</i>
A	voltage and time	charge and voltage	current and time
B	current and time	voltage and time	charge and voltage
C	current and time	charge and voltage	voltage and time
D	voltage and time	current and time	charge and voltage
E	charge and voltage	current and time	voltage and time